



华南理工大学  
South China University of Technology

# 课程设计报告书

# 基于 VHDL 的万年历系统设计

## 目录

一、选题背景	1
1.1 验收标准	1
1.2 设计思想	1
二、方案论证	1
三、过程论述	2
3.1 整体设计	2
3.1.1 设计思路	2
3.1.2 整体流程图	2
3.2 各模块设计分析	3
3.2.1 计数器模块分析	3
3.2.2 设置模块	12
3.2.3 显示切换模块	14
3.2.4 数码管驱动模块	15
3.2.5 闹钟模块	21
3.2.6 流水灯模块	25
3.2.7 延时去抖模块	26
3.3 整机电路图	28
四、结果分析	26
4.1 仿真结果及分析	29
4.1.1 秒计数器模块	29
4.1.2 分计数器模块	29
4.1.3 时计数器模块	29
4.1.4 日计数器模块	30
4.1.5 月计数器模块	30
4.1.6 年计数器模块	31
4.1.7 设置模块	31
4.1.8 闹钟模块	33
4.2 实验验证	33
五、课程设计总结	37

## 一、选题背景

### 1.1 验收标准：

设计一个万年历系统，通过数码管显示。

- (1) 数码管显示时间信息，包括年、月、日、时、分、秒。
- (2) 数码管开始显示时分秒，通过按键切换显示年月日。
- (3) 按键设置时间，通过选择时间单位，增加的方式设置。
- (4) 具有闹钟功能，闹钟设置方式同时间设置方式。
- (5) 有走马灯功能。

### 1.2 设计思想：

这次设计是基于 VHDL 语言进行的，设计过程中，采用了模块化的思想，实现各个功能的设计。根据验收标准，把万年历分成计时模块、显示模块、时间设置模块、闹钟模块。

万年历有计时模式和闹钟模式，通过按键切换。在计时模式下，计时模块利用了 VHDL 分频计数原理，根据年月日时分秒设计不同进制的计数器进行计时进位。由于只有 8 个数码管，无法显示所有信息，所以显示模块中把年月日和时分秒分开显示，通过按键切换。时间设置模块需要 2 个按键进行控制，一个按键选择当前显示的时间中的一位，另一个按键改变时间。闹钟模式是计时模式的延伸，通过两个按键设置小时和分钟，一个按键复位，完成特定闹钟设置。在闹钟模式下，计时照常进行，完成闹钟设置后，到达设定时间，蜂鸣器会发出警报声，有流水灯提醒。

由于设计中多处使用到按键，所以加上延时去抖代码。在整体设计过程中，多处需要选择判断，可以通过 VHDL 中的 case 语句或 if 语句来实现。

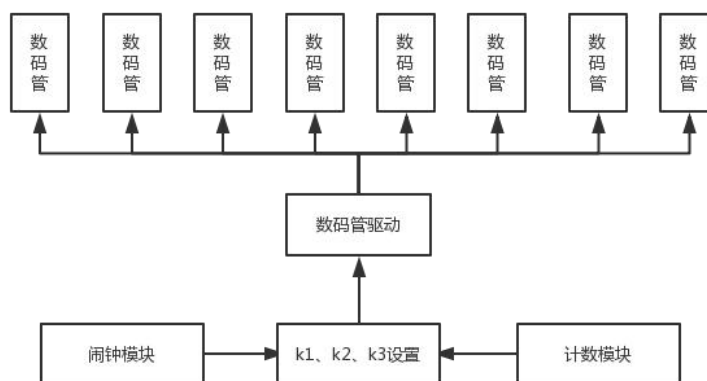


图 1 计时器运行流程图

## 二、方案论证(设计理念)

本次设计利用 VHDL 分频计数原理，对时间进行计数，根据秒到年不同进制进行设计，时间相对更精确。设计过程中利用 VHDL 中的 case 语句和 if 语句进行选择，逻辑清晰，代码可读性强，有利于后期维护。显示模块由于数码管数量限制，采用分开显示的方式，

是切实可行的。同时，由于使用了按键，加上延时去抖的模块，使之更稳定，减少使用误操作的概率。外接蜂鸣器模块，用于闹钟的提醒。走马灯功能也用在闹钟提醒里。

### 三、过程论述

#### 3.1 整体设计

##### 3.1.1 设计思路

万年历有计时模式和闹钟模式，通过按键 k0 进行切换，两种模式下，计时模块都照常进行。通过 led 灯 1、2、3 来显示当前状态。

计时模块根据时间不同包括了分频、秒、分、时、日、月、年模块。分频器采用系统 50MHz 信号，每记录 50M 次输出，即输出 1 秒。秒、分模块采用 60 进制计数器，时采用 24 进制计数器，月采用 12 进制计数器，年分高位和低位采用 100 进制计数器。而日模块，根据大月（1、3、5、7、8、10、12）和小月（4、6、9、11）和闰年二月和平年二月分别采用 31 进制、30 进制、29 进制、28 进制计数器，通过一个选择器对年份、月份信息判断选择相应计数器。同时除年高位外每个计数器都有进位输出，以实现低位时间单位向高一级的时间单位进位。

时间设置功能，按键 k1 选择要改变的时间单位，按键 k2 加 1，以实现设置时间。设置功能只改变年月日时分五个时间六个状态（年分高低位），通过 led 灯 1、2、3 来表示当前状态。

受硬件设备所限，在显示模块中，开始显示时分秒，按下 k3，显示年月日。

闹钟模块中，通过按键来控制时间，对 k1、k2、k3 按键实现复用，k1、k2 分别设置小时、分钟，k3 复位，完成设置后按 k0 退出。当系统时间和闹钟设置时间一致，闹钟会发出提醒。闹钟模块外接蜂鸣器，同时用 led 灯 4、5、6 作为流水灯，用于提醒。

##### 3.1.2 整体流程图

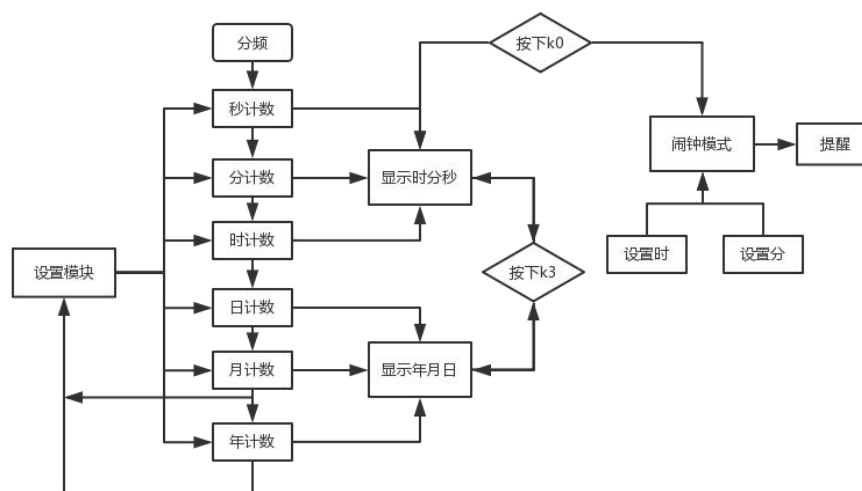


图 2 整体流程图

### 3.2 各模块设计分析

#### 3.2.1 计数器模块

##### (1) 分频模块

系统采用 50MHz 的信号，分频器每记录脉冲 50M 次输出，实现输出周期为 1 秒的信号，作为秒计数器的输入。

 


图 3 分频模块图

代码如下：

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY clkdiv IS
PORT(CLK:IN STD_LOGIC;Q:OUT STD_LOGIC);
END clkdiv;
ARCHITECTURE BEHAV OF clkdiv IS
BEGIN
PROCESS(CLK)
VARIABLE TIME:INTEGER RANGE 0 TO 500000000;
BEGIN
    IF RISING_EDGE(CLK) THEN
        TIME:=TIME+1;
        IF TIME=250000000 THEN
            Q<='1';
        ELSIF TIME=500000000 THEN
            Q<='0';
            TIME:=0;
        END IF;
    END IF;
END PROCESS;
END BEHAV;
```

## (2) 秒计数器模块

秒计数器为 60 进制计数器，clk 有时钟输入时，计数器计数，q 口输出为当前计数，输出到显示模块，c 为进位输出，当计数到达 60 时，计数置零，同时 c 口输出。

 


图 4 秒计数器模块图

代码如下：

```
Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity second is
Port(clk,reset:in std_logic;
      q:out std_logic_vector(7 downto 0);
      c:out std_logic);
end entity;
architecture behav of second is
begin
process(clk)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='0' then r:="00000000";
    elsif (rising_edge(clk)) then
        r:=r+1;c<='0';
        if r(3 downto 0)="1010" then
            r(3 downto 0):="0000";
            if r(7 downto 4)/="0101" then
                r(7 downto 4):=r(7 downto 4)+1;
            elsif r(7 downto 4)="0101" then
                r(7 downto 4):="0000";c<='1';
            end if;
        end if;
    end if;
end if;
q<=r;
```

```

end process;
end behav;

```

### (3) 分计数器模块

分计数器也为 60 进制计数器，同秒计数器。

 


图 5 分计数器模块图

代码如下：

```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity minute is
Port(clk,reset:in std_logic;
      q:out std_logic_vector(7 downto 0);
      c:out std_logic);
end entity;
architecture behav of minute is
begin
process(clk)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='0' then r:="00000000";
    elsif (rising_edge(clk)) then
        r:=r+1;c<='0';
        if r(3 downto 0)="1010" then
            r(3 downto 0):="0000";
            if r(7 downto 4)/="0101" then
                r(7 downto 4):=r(7 downto 4)+1;
            elsif r(7 downto 4)="0101" then
                r(7 downto 4):="0000";c<='1';
            end if;
        end if;
    end if;
end if;

```

```

        end if;
        q<=r;
    end process;
end behav;

```

(4) 时计数器模块

时计数器为 24 进制计数器，其它同秒计数器。

 


图 6 时计数器模块图

代码如下：

```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity hour is
Port(clk,reset:in std_logic;
      q:out std_logic_vector(7 downto 0);
      c:out std_logic);
end entity;
architecture behav of hour is
begin
process(clk,reset)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='0' then r:="00000000";
    elsif (rising_edge(clk)) then
        r:=r+1;c<='0';
        if r(3 downto 0)=4 and r(7 downto 4)=2 then
            r(3 downto 0):="0000";r(7 downto 4):="0000";c<='1';
        elsif r(3 downto 0)=10 then
            r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;
        end if;
    end if;
    q<=r;
end process;

```



```

end process;
end behav;

```

#### (5) 日计数器模块

当有时钟输入 clk 口时，日计数器要根据 sel 输入判断日计数器的进制，包括大月 31 进制、小月 30 进制、闰年二月 29 进制、平年二月 28 进制。计数方式同上。

 


图 7 日计数器模块

代码如下：

```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity day is
Port(clk,reset:in std_logic;
      sel:in std_logic_vector(1 downto 0);
      q:out std_logic_vector(7 downto 0);
      c:out std_logic);
end entity;
architecture behav of day is
begin
process(clk,reset)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='0' then r:="00000001";
    elsif (rising_edge(clk)) then
        r:=r+1;c<='0';
        case sel is
            when "00"=>
                if r(3 downto 0)=2 and r(7 downto 4)=3 then
                    r(3 downto 0):="0001";r(7 downto 4):="0000";c<='1';
                elsif r(3 downto 0)=10 then
                    r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;

```

```

        end if;
    when "01" =>
        if r(3 downto 0)=1 and r(7 downto 4)=3 then
            r(3 downto 0):="0001";r(7 downto 4):="0000";c<='1';
        elsif r(3 downto 0)=10 then
            r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;
        end if;
    when "10" =>
        if r(3 downto 0)=10 and r(7 downto 4)=2 then
            r(3 downto 0):="0001";r(7 downto 4):="0000";c<='1';
        elsif r(3 downto 0)=10 then
            r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;
        end if;
    when "11" =>
        if r(3 downto 0)=9 and r(7 downto 4)=2 then
            r(3 downto 0):="0001";r(7 downto 4):="0000";c<='1';
        elsif r(3 downto 0)=10 then
            r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;
        end if;
    when others=>null;
end case;
end if;
q<=r;
end process;
end behav;

```

#### (6) 月计数器模块

时钟到来时，月计数器根据 run 输入判断是否为闰年，然后根据计数信息，通过 sel 把信息发给日计数器。计数方式同上。

 


图8 月计数器模块图

代码如下:

```
Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity month is
Port(clk,reset:in std_logic;
      run:in std_logic;--runnian wei 1
      sel:out std_logic_vector(1 downto 0);
      q:out std_logic_vector(7 downto 0);
      c:out std_logic);
end entity;
architecture behav of month is
begin
process(clk,run,reset)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='0' then r:="00000001";
    elsif (rising_edge(clk)) then
        r:=r+1;c<='0';
        if r(3 downto 0)=3 and r(7 downto 4)=1 then
            r(3 downto 0):="0001";r(7 downto 4):="0000";c<='1';
        elsif r(3 downto 0)=10 then
            r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;
        end if;
    end if;
    case r is
        when "00000001"=>sel<="00";
        when "00000010"=>sel<="11";
            if(run='1')then sel<="10";
        end if;
        when "00000011"=>sel<="00";
        when "00000100"=>sel<="01";
        when "00000101"=>sel<="00";
        when "00000110"=>sel<="01";
        when "00000111"=>sel<="00";
        when "00001000"=>sel<="00";
```

```

        when "00001001"=>sel<="01";
        when "00001010"=>sel<="00";
        when "00001011"=>sel<="01";
        when "00001100"=>sel<="00";
        when others=>null;
    end case;
    q<=r;
end process;
end behav;

```

### (7) 年计数器模块

年计数器分为置年高位和低位两种模式，由输入 uph 口控制。根据自身计数判断是否为闰年，通过 run 口输入到月计数器中。当处于置低位模式，每次计数加 1，当处于置高位模式，每次计数加 100。其它计数方式同上。

 


图9 年计数模块

代码如下：

```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity year is
Port(clk,reset,uph:in std_logic;
      qh:out std_logic_vector(7 downto 0);
      ql:out std_logic_vector(7 downto 0);
      run:out std_logic);
end entity;
architecture behav of year is
begin
process(clk,reset)
variable r:std_logic_vector(15 downto 0);
variable a:integer range 1 to 4;
variable b:integer range 1 to 100;

```

```

variable c:integer range 1 to 400;
begin
    if reset='0' then r:="0010000000000000";
    elsif (rising_edge(clk)) then
        a:=a+1;b:=b+1;c:=c+1;run<='0';
        if uph='1' then r(11 downto 8):=r(11 downto 8)+1;
            if r(11 downto 8)="1010" then
                r(11 downto 8):="0000";
                r(15 downto 12):=r(15 downto 12)+1;
            end if;
        else r:=r+1;
        end if;
        if a=4 then run<='1';a:=1;
        end if;
        if b=100 then run<='0';b:=1;
        end if;
        if c=100 then run<='1';c:=1;
        end if;
        if r(3 downto 0)="1010" then
            r(3 downto 0):="0000";
            r(7 downto 4):=r(7 downto 4)+1;
            if r(7 downto 4)="1010" then
                r(7 downto 4):="0000";
                r(15 downto 8):=r(15 downto 8)+1;
                if r(11 downto 8)="1010" then
                    r(11 downto 8):="0000";
                    r(15 downto 12):=r(15 downto 12)+1;
                end if;
            end if;
        end if;
        if r=9999 then
            r:="0000000000000000";
        end if;

    end if;
    qh<=r(15 downto 8);

```

```

        ql<=r(7 downto 0);
end process;
end behav;

```

### 3.2.2 设置模块

设置模块通过 case 语句实现。k1 选择输入模式，包括正常显示、置分、置时、置日、置月、置年高低位其中模式，通过 led 灯 1、2、3 亮灭表示当前所处状态。选择好时间后，每按下 k2 一次就加 1，以完成时间的设置。

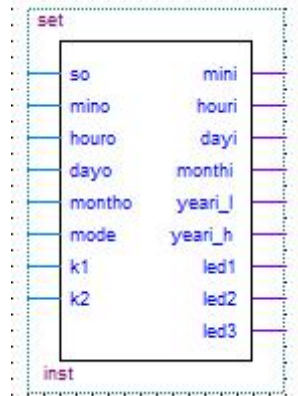


图 10 设置模块图

代码如下：

```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity set is
Port( so,mino,houro,dayo,montho:in std_logic;
      mode:in std_logic;
      k1,k2:in std_logic;
      mini,houri,dayi,monthi,yeari_l,yeari_h:out std_logic;
      led1,led2,led3:out std_logic);
end entity;
architecture behav of set is
    signal r:std_logic_vector(2 downto 0);
begin
    process(mode,k1,k2,so,mino,houro,dayo,montho)
    begin
        case mode is
            when '0' =>
                if k1'event and k1='1' then
                    r<=r+'1';

```

```

        if r=6 then
            r<="000";
        end if;
    end if;
    yeari_l<='0';
    yeari_h<='0';
    case r is
        when "000"=>mini<=so;houri<=mino;dayi<=      houro;monthi<=
dayo;yeari_l<= montho;

            led1<='0';led2<='0';led3<='0';
        when "001"=>mini<=k2;houri<='0'; dayi<='0';   monthi<='0';
            led1<='0';led2<='0';led3<='1';
        when "010"=>mini<=so;houri<=k2;  dayi<='0';   monthi<='0';
            led1<='0';led2<='1';led3<='0';
        when "011"=>mini<=so;houri<=mino;dayi<=k2;    monthi<='0';
            led1<='0';led2<='1';led3<='1';
        when "100"=>mini<=so;houri<=mino;dayi<= houro;monthi<=k2;
            led1<='1';led2<='0';led3<='0';
        when "101"=>mini<=so;houri<=mino;dayi<=
houro;monthi<=dayo;yeari_l<=k2;
            led1<='1';led2<='0';led3<='1';
        when "110"=>mini<=so;houri<=mino;dayi<=
houro;monthi<=dayo;yeari_l<=k2;yeari_h<='1';
            led1<='1';led2<='1';led3<='0';

        when others=>null;
    end case;
when '1'=>
    r<="000";
    mini<=so;
    houri<=mino;
    dayi<= houro;
    monthi<= dayo;
    yeari_l<= montho;
    led1<='1';
    led2<='1';

```

```

        led3<='1';
    end case;
end process;
end behav;

```

### 3.2.3 显示切换模块

由于只有 8 个数码管，年月日和时分秒要分开显示，通过按键 k3 切换显示。

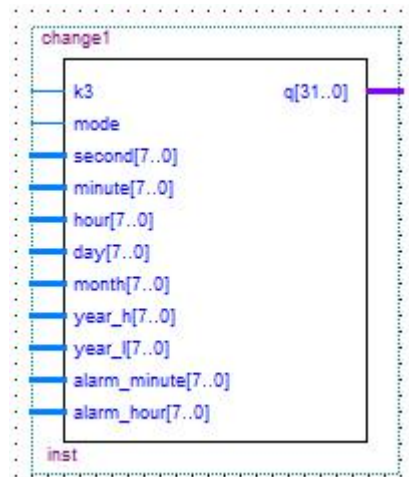


图 11 显示切换模块

代码如下：

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity changel is
port(k3:in std_logic;
    mode:in std_logic;
    second:in std_logic_vector(7 downto 0);
    minute:in std_logic_vector(7 downto 0);
    hour:in std_logic_vector(7 downto 0);
    day:in std_logic_vector(7 downto 0);
    month:in std_logic_vector(7 downto 0);
    year_h:in std_logic_vector(7 downto 0);
    year_l:in std_logic_vector(7 downto 0);
    alarm_minute:in std_logic_vector(7 downto 0);
    alarm_hour:in std_logic_vector(7 downto 0);
    q:out std_logic_vector(31 downto 0));
end entity;

```



```

architecture behav of changel is
    signal key_value:std_logic_vector(1 downto 0);
begin
    process(k3)
    begin
        if(k3'event and k3='1') then
            key_value<=key_value+'1';
            if key_value="01" then
                key_value<="00";
            end if;
        end if;
    end process;
end process;

```

```

process(mode, key_value, second, minute, hour, day, month, year_h, year_l, alarm_hour, alarm_minute)
begin
    case mode is
        when '0' =>
            if key_value="00" then
                q<="00000000"&hour&minute&second;
            else
                q<=year_h&year_l&month&day;
            end if;
        when '1' =>
            q<="00000000"&alarm_hour&alarm_minute&"00000000";
    end case;
end process;
end behav;

```

### 3.2.4 数码管驱动模块



图 12 数码管驱动模块

代码如下:

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
use IEEE.STD_LOGIC_unsigned.all;
ENTITY seg IS
    PORT(clk:IN std_logic;
          idata:IN std_logic_vector(31 downto 0);
          ds_stcp,ds_shcp,ds_data:OUT std_logic);
END entity;
ARCHITECTURE behav OF seg IS
    signal b,clk2,ds_stcpr,ds_shcpr,ds_datar:std_logic;
    signal cnt: std_logic_vector(11 DOWNT0 0);
    signal seg_duan :std_logic_vector(7 downto 0);
    signal seg_wei :std_logic_vector(7 downto 0);
    signal seg_num:std_logic_vector(3 downto 0);
    signal sel:std_logic_vector(2 downto 0);
    --signal idata: std_logic_vector(31 DOWNT0 0);

    CONSTANT SEG_NUM0:std_logic_vector(7 downto 0):="11000000";
    CONSTANT SEG_NUM1:std_logic_vector(7 downto 0):="11111001";
    CONSTANT SEG_NUM2:std_logic_vector(7 downto 0):="10100100";
    CONSTANT SEG_NUM3:std_logic_vector(7 downto 0):="10110000";
    CONSTANT SEG_NUM4:std_logic_vector(7 downto 0):="10011001";
    CONSTANT SEG_NUM5:std_logic_vector(7 downto 0):="10010010";
    CONSTANT SEG_NUM6:std_logic_vector(7 downto 0):="10000010";
    CONSTANT SEG_NUM7:std_logic_vector(7 downto 0):="11111000";
    CONSTANT SEG_NUM8:std_logic_vector(7 downto 0):="10000000";
    CONSTANT SEG_NUM9:std_logic_vector(7 downto 0):="10010000";

    CONSTANT SEG_WE0:std_logic_vector(7 downto 0):="11111110";
    CONSTANT SEG_WE1:std_logic_vector(7 downto 0):="11111101";
    CONSTANT SEG_WE2:std_logic_vector(7 downto 0):="11111011";
    CONSTANT SEG_WE3:std_logic_vector(7 downto 0):="11110111";
    CONSTANT SEG_WE4:std_logic_vector(7 downto 0):="11101111";
    CONSTANT SEG_WE5:std_logic_vector(7 downto 0):="11011111";
    CONSTANT SEG_WE6:std_logic_vector(7 downto 0):="10111111";
```

```
CONSTANT SEG_WE7:std_logic_vector(7 downto 0):="01111111";
```

```
BEGIN
```

```
    process(clk)
```

```
    begin
```

```
        if(clk'event and clk='1') then
```

```
            clk2<='0';
```

```
            clk2<=not clk2;
```

```
        end if;
```

```
    end process;
```

```
    process(clk2, sel, seg_num)
```

```
    begin
```

```
        if(clk2'event and clk2='1') then
```

```
            cnt<=cnt+1;
```

```
            if(
                (cnt >= x"002" and cnt < x"022") or (cnt >= x"024" and cnt < x"044")
                or (cnt >= x"046" and cnt < x"066") or (cnt >= x"068" and cnt < x"088")
                or (cnt >= x"08a" and cnt < x"0aa") or (cnt >= x"0ac" and cnt < x"0cc")
                or (cnt >= x"0ce" and cnt < x"0ee") or (cnt >= x"0f0" and cnt < x"110")
                or (cnt >= x"112" and cnt < x"132") or (cnt >= x"134" and cnt < x"154")
                or (cnt >= x"156" and cnt < x"176") or (cnt >= x"178" and cnt < x"198")
                or (cnt >= x"19a" and cnt < x"1ba") or (cnt >= x"1bc" and cnt < x"1dc")
                or (cnt >= x"1de" and cnt < x"1fe")
            )
```

```
        )
```

```
        then
```

```
            ds_shcpr<=not ds_shcpr ;
```

```
        else ds_shcpr<='0';
```

```
        end if;
```

```
        if( (cnt = x"001") or (cnt = x"023")
```

```
            or (cnt = x"045") or (cnt = x"067")
```

```
            or (cnt = x"089") or (cnt = x"0ab")
```

```
            or (cnt = x"0cd") or (cnt = x"0ef")
```

```
            or (cnt = x"111") or (cnt = x"133")
```

```
            or (cnt = x"155") or (cnt = x"177")
```

```

        or (cnt = x"199") or (cnt = x"1bb")
        or (cnt = x"1dd") or (cnt = x"199")
    ) then
        ds_stcpr<='0';
    end if;

if( (cnt = x"022") or (cnt = x"044")
    or (cnt = x"066") or (cnt = x"088")
    or (cnt = x"0aa") or (cnt = x"0cc")
    or (cnt = x"0ee") or (cnt = x"110")
    or (cnt = x"132") or (cnt = x"154")
    or (cnt = x"176") or (cnt = x"198")
    or (cnt = x"1ba") or (cnt = x"1dc")
    or (cnt = x"1fe")
    ) then
        ds_stcpr<='1';
    end if;

if (cnt=x"200")then
    cnt<=x"000";
    end if;
end if;
sel<=cnt(8 downto 6);
case sel is
    when "000" => seg_wei<=seg_we0;seg_num<=idata(3 downto 0);
    when "001" => seg_wei<=seg_we1;seg_num<=idata(7 downto 4);
    when "010" => seg_wei<=seg_we2;seg_num<=idata(11 downto 8 );
    when "011" => seg_wei<=seg_we3;seg_num<=idata(15 downto 12);
    when "100" => seg_wei<=seg_we4;seg_num<=idata(19 downto 16);
    when "101" => seg_wei<=seg_we5;seg_num<=idata(23 downto 20);
    when "110" => seg_wei<=seg_we6;seg_num<=idata(27 downto 24);
    when "111" => seg_wei<=seg_we7;seg_num<=idata(31 downto 28);
    when others=>NULL;
end case;

case seg_num is
    when "0000" =>seg_duan <= SEG_NUM0;
    when "0001" =>seg_duan <= SEG_NUM1;

```

```

when "0010" =>seg_duan <= SEG_NUM2;
when "0011" =>seg_duan <= SEG_NUM3;
when "0100" =>seg_duan <= SEG_NUM4;
when "0101" =>seg_duan <= SEG_NUM5;
when "0110" =>seg_duan <= SEG_NUM6;
when "0111" =>seg_duan <= SEG_NUM7;
when "1000" =>seg_duan <= SEG_NUM8;
when "1001" =>seg_duan <= SEG_NUM9;
when others=>NULL;
end case;
end process;
process(cnt)
begin
    case cnt is
        when x"002"|x"046"|x"08a"|x"0ce"|x"112"|x"156"|x"19a"|x"1de" => ds_datar
<= seg_duan(7);
        when x"004"|x"048"|x"08c"|x"0d0"|x"114"|x"158"|x"19c"|x"1e0" => ds_datar
<= seg_duan(6);
        when x"006"|x"04a"|x"08e"|x"0d2"|x"116"|x"15a"|x"19e"|x"1e2" => ds_datar
<= seg_duan(5);
        when x"008"|x"04c"|x"090"|x"0d4"|x"118"|x"15c"|x"1a0"|x"1e4" => ds_datar
<= seg_duan(4);
        when x"00a"|x"04e"|x"092"|x"0d6"|x"11a"|x"15e"|x"1a2"|x"1e6" => ds_datar
<= seg_duan(3);
        when x"00c"|x"050"|x"094"|x"0d8"|x"11c"|x"160"|x"1a4"|x"1e8" => ds_datar
<= seg_duan(2);
        when x"00e"|x"052"|x"096"|x"0da"|x"11e"|x"162"|x"1a6"|x"1ea" => ds_datar
<= seg_duan(1);
        when x"010"|x"054"|x"098"|x"0dc"|x"120"|x"164"|x"1a8"|x"1ec" => ds_datar
<= seg_duan(0);
        when x"012"|x"056"|x"09a"|x"0de"|x"122"|x"166"|x"1aa"|x"1ee" => ds_datar
<= seg_wei(0);
        when x"014"|x"058"|x"09c"|x"0e0"|x"124"|x"168"|x"1ac"|x"1f0" => ds_datar
<= seg_wei(1);
        when x"016"|x"05a"|x"09e"|x"0e2"|x"126"|x"16a"|x"1ae"|x"1f2" => ds_datar
<= seg_wei(2);

```

```

        when x"018"|x"05c"|x"0a0"|x"0e4"|x"128"|x"16c"|x"1b0"|x"1f4" => ds_datar
<= seg_wei(3);
        when x"01a"|x"05e"|x"0a2"|x"0e6"|x"12a"|x"16e"|x"1b2"|x"1f6" => ds_datar
<= seg_wei(4);
        when x"01c"|x"060"|x"0a4"|x"0e8"|x"12c"|x"170"|x"1b4"|x"1f8" => ds_datar
<= seg_wei(5);
        when x"01e"|x"062"|x"0a6"|x"0ea"|x"12e"|x"172"|x"1b6"|x"1fa" => ds_datar
<= seg_wei(6);
        when x"020"|x"064"|x"0a8"|x"0ec"|x"130"|x"174"|x"1b8"|x"1fc" => ds_datar
<= seg_wei(7);

```

```

        when x"024"|x"068"|x"0ac"|x"0f0"|x"134"|x"178"|x"1bc" => ds_datar <= '1';
        when x"026"|x"06a"|x"0ae"|x"0f2"|x"136"|x"17a"|x"1be" => ds_datar <= '1';
        when x"028"|x"06c"|x"0b0"|x"0f4"|x"138"|x"17c"|x"1c0" => ds_datar <= '1';
        when x"02a"|x"06e"|x"0b2"|x"0f6"|x"13a"|x"17e"|x"1c2" => ds_datar <= '1';
        when x"02c"|x"070"|x"0b4"|x"0f8"|x"13c"|x"180"|x"1c4" => ds_datar <= '1';
        when x"02e"|x"072"|x"0b6"|x"0fa"|x"13e"|x"182"|x"1c6" => ds_datar <= '1';
        when x"030"|x"074"|x"0b8"|x"0fc"|x"140"|x"184"|x"1c8" => ds_datar <= '1';
        when x"032"|x"076"|x"0ba"|x"0fe"|x"142"|x"186"|x"1ca" => ds_datar <= '1';
        when x"034"|x"078"|x"0bc"|x"100"|x"144"|x"188"|x"1cc" => ds_datar <= '1';
        when x"036"|x"07a"|x"0be"|x"102"|x"146"|x"18a"|x"1ce" => ds_datar <= '1';
        when x"038"|x"07c"|x"0c0"|x"104"|x"148"|x"18c"|x"1d0" => ds_datar <= '1';
        when x"03a"|x"07e"|x"0c2"|x"106"|x"14a"|x"18e"|x"1d2" => ds_datar <= '1';
        when x"03c"|x"080"|x"0c4"|x"108"|x"14c"|x"190"|x"1d4" => ds_datar <= '1';
        when x"03e"|x"082"|x"0c6"|x"10a"|x"14e"|x"192"|x"1d6" => ds_datar <= '1';
        when x"040"|x"084"|x"0c8"|x"10c"|x"150"|x"194"|x"1d8" => ds_datar <= '1';
        when x"042"|x"086"|x"0ca"|x"10e"|x"152"|x"196"|x"1da" => ds_datar <= '1';
        when others=>ds_datar<='0';

```

```

    end case;

```

```

end process;

```

```

    ds_stcp<=ds_stcpr;

```

```

    ds_shcp<=ds_shcpr;

```

```

    ds_data<=ds_datar;

```

```

end behav;

```

### 3.2.5 闹钟模块

#### (1) 闹钟设置模块

mode 有输入时，系统进入闹钟模式，k1、k2、k3 按键功能改变。闹钟模式下，k1 设置小时，k2 设置分钟，k3 置零完成。

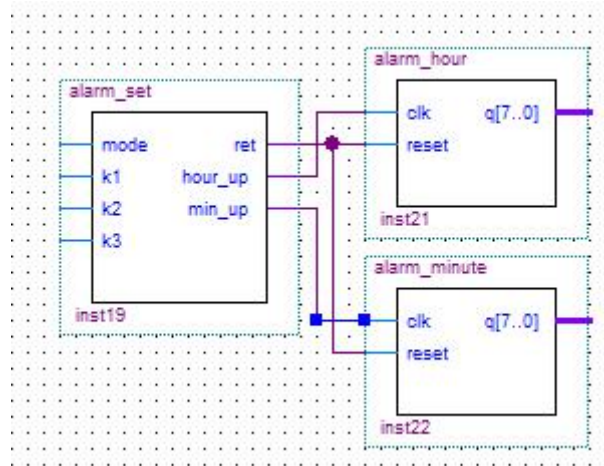


图 13 闹钟设置模块

代码如下：

```
Library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
Entity alarm_set is
Port( mode:in std_logic;
      k1,k2,k3:in std_logic;
      ret:out std_logic;
      hour_up,min_up:out std_logic);
end entity;
architecture behav of alarm_set is
begin
  process(mode,k1,k2,k3)
  begin
    case mode is
      when '1' =>
        if k1='1' then
          hour_up<='1';
        else hour_up<='0';
        end if;
        if k2='1' then
```

```

        min_up<='1' ;
    else min_up<='0' ;
    end if;
    if k3='1' then
        ret<='1' ;
    else ret<='0' ;
    end if;
when '0' =>
    hour_up<='0' ;
    min_up<='0' ;
    ret<='0' ;
end case;
end process;
end behav;

```

```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity alarm_hour is
Port(clk,reset:in std_logic;
      q:out std_logic_vector(7 downto 0));
end entity;
architecture behav of alarm_hour is
begin
process(clk)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='1' then r:="00000000";
    elsif (rising_edge(clk)) then
        r:=r+1;
        if r(3 downto 0)=4 and r(7 downto 4)=2 then
            r(3 downto 0):="0000";r(7 downto 4):="0000";
        elsif r(3 downto 0)=9 then
            r(3 downto 0):="0000";r(7 downto 4):=r(7 downto 4)+1;
        end if;
    end if;
end if;

```



```

        q<=r;
end process;
end behav;

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity alarm_minute is
Port(clk,reset:in std_logic;
      q:out std_logic_vector(7 downto 0));
end entity;
architecture behav of alarm_minute is
begin
process(clk)
variable r:std_logic_vector(7 downto 0);
begin
    if reset='1' then r:="00000000";
    elsif (rising_edge(clk)) then
        r:=r+1;
        if r(3 downto 0)="1010" then
            r(3 downto 0):="0000";
            if r(7 downto 4)/="0101" then
                r(7 downto 4):=r(7 downto 4)+1;
            elsif r(7 downto 4)="0101" then
                r(7 downto 4):="0000";
            end if;
        end if;
    end if;
end if;
q<=r;
end process;
end behav;

```

## (2) 闹钟提醒模块

当计时模式下的时间和闹钟设置的时间一致时，闹钟提醒用户。

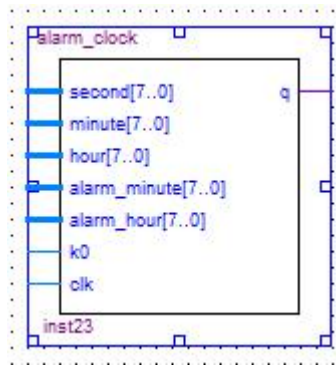


图 14 闹钟提醒模块

代码如下：

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
Entity alarm_clock is
Port( second:in std_logic_vector(7 downto 0);
      minute:in std_logic_vector(7 downto 0);
      hour:in std_logic_vector(7 downto 0);
      alarm_minute:in std_logic_vector(7 downto 0);
      alarm_hour:in std_logic_vector(7 downto 0);
      k0:in std_logic;
      clk:in std_logic;
      q:out std_logic);
end entity;
architecture behav of alarm_clock is
begin
  process(clk)
  begin
    if(clk'event and clk='1') then
      if(k0='1') then
        q<='0';
      elsif(hour=alarm_hour) then
        if(minute=alarm_minute) then
          if(second="0000000") then
            q<='1';
          end if;
        end if;
      end if;
    end if;
  end process;
end architecture;
```

```

        end if;
    end if;
end process;
end behav;

```

### 3.2.6 流水灯模块

当时钟到来时，led 灯 4、5、6 轮流点亮，形成流水灯，用于闹钟的提醒。

 


图 14 流水灯模块

代码如下：

```

LIBRARY IEEE;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
ENTITY light IS
    PORT(clk,start:IN std_logic;
          LED:OUT std_logic_vector(2 DOWNTO 0));
END light;
ARCHITECTURE Behav OF light IS
    signal i:std_logic_vector(1 DOWNTO 0);
    signal c: std_logic;
    signal count:integer range 0 to 5000000;
BEGIN

    process(clk)
    begin
        if (rising_edge(clk))then
            count<=count+1;
            if count=2500000 then
                c<='1';
            elsif count=5000000 then
                c<='0';
                count<=0;
            end if;
        end if;
    end process;

```

```

        end if ;
    end if;
end process;

PROCESS(c, start)
BEGIN
    IF(start='0') THEN
        LED<="000"; i<="00";
    ELSIF(c' EVENT AND c='1') THEN
        IF(i=2) THEN
            i<="00";
        ELSE
            i<=i+'1';
        END IF;
    CASE i IS
        WHEN "00"=>LED<="110";
        WHEN "01"=>LED<="101";
        WHEN "10"=>LED<="011";
        WHEN others=>LED<="111";
    END CASE;
    END IF;
END PROCESS;
END Behav;

```

### 3.2.7 延时去抖模块

延时去抖模块根据按下按键时长判断此次输入是否有效，保证按键输入的有效性。

 


图 15 延时去抖模块

代码如下：

```

LIBRARY IEEE ;
USE IEEE.std_logic_1164.all ;
USE IEEE.std_logic_unsigned.all ;
ENTITY key_read IS

```

```

PORT (clk : IN std_logic ;
sw :IN std_logic ;
low_sw_an:out std_logic);
END ENTITY ;

ARCHITECTURE behav OF key_read IS
SIGNAL key_rst : std_logic ;
SIGNAL key_rst_an : std_logic ;
SIGNAL key_rst_r :std_logic ;
SIGNAL low_sw : std_logic ;
SIGNAL low_sw_r :std_logic ;
SIGNAL cnt : std_logic_vector (19 downto 0) ;
BEGIN
PROCESS (clk)
BEGIN
IF clk'event and clk = '1' THEN
key_rst <= sw;
END IF ;
END PROCESS ;
PROCESS (clk)
BEGIN
IF clk'event and clk = '1' THEN
key_rst_r <= key_rst ;
END IF ;
END PROCESS ;
key_rst_an <= key_rst_r AND NOT key_rst ;
PROCESS (clk )
BEGIN
IF clk'event and clk = '1' THEN
IF key_rst_an = '0'
THEN cnt <= cnt + '1' ;
ELSE cnt <= (OTHERS => '0') ;
END IF ;
END IF ;
END PROCESS ;
PROCESS (clk)
BEGIN

```

```

IF clk'event and clk = '1' THEN
IF cnt = "11111111111111111111" THEN
low_sw <= sw;
ELSE NULL ;
    END IF ;
END IF ;
END PROCESS ;
PROCESS (clk )
BEGIN
IF clk'event and clk = '1' THEN
low_sw_r <= low_sw ;
END IF ;
END PROCESS ;
low_sw_an <= low_sw_r AND NOT low_sw ;
END behav;

```

### 3.3 整机电路图

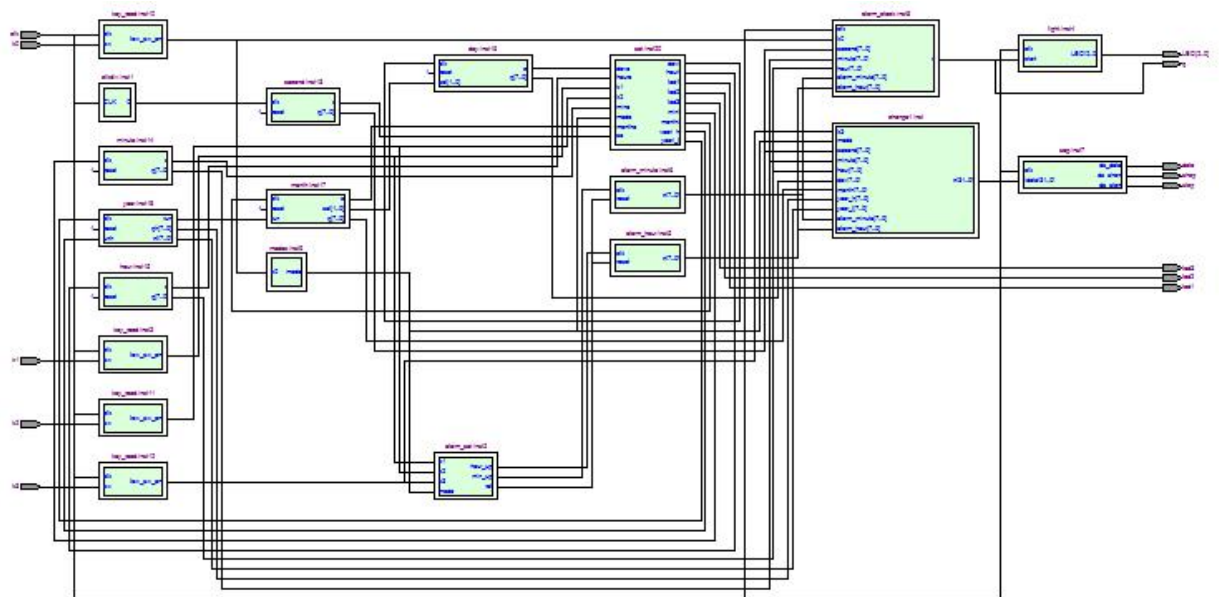


图 16 整机电路图

## 四、结果分析

### 4.1 仿真结果及分析

#### 4.1.1 秒计数器模块:

 


图 17 秒计数器模块仿真图

由上图可以看出，在秒计数器模块中每计数 60 次产生一个进位，设计正确。

#### 4.1.2 分计数器模块:

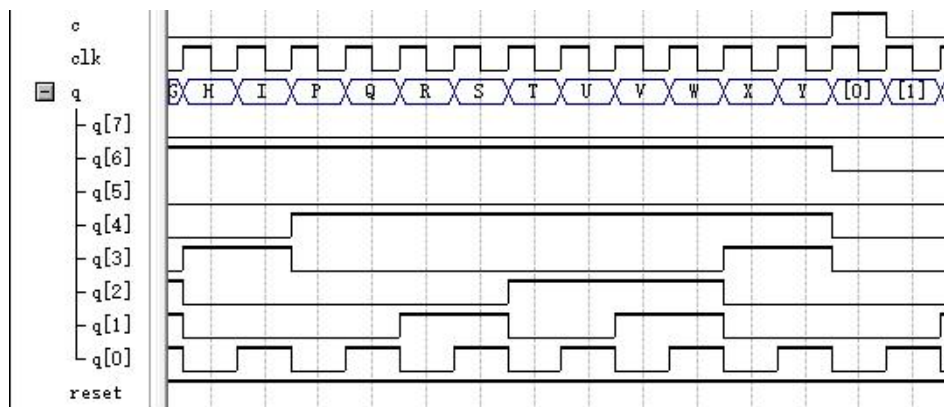


图 18 分计数器模块仿真图

由上图可以看出，在分计数器模块中每计数 60 次产生一个进位，设计正确。

#### 4.1.3 时计数器模块:

 


图 19 时计数器模块仿真图

由上图可以看出，在时计数器模块中每计数 24 次产生一个进位，设计正确。

4.1.4 日计数器模块

 


图 20 日计数器模板仿真图（大月）

 


图 21 日计数器模板仿真图（小月）

 


图 21 日计数器模板仿真图（闰年 2 月）

 


图 23 日计数器模板仿真图（平年 2 月）

由上面仿真图可以看出，根据不同 sel 输入，日计数器有不同的进制，来表示大月、小月、闰年 2 月、平年 2 月的天数。

4.1.5 月计数器模块

 


图 24 月计数器模板仿真图（平年）



 


图 25 月计数器模板仿真图（闰年）

由上面仿真图可以看出，月计数器为 12 进制计数器，同时，不同月份的 sel 输出不同，run 输入影响了 2 月份 sel 输出，所以设计正确。

#### 4.1.6 年计数器模块

 


图 26 年计数器模板仿真图

由上图可以看出，uph 控制年高位还是年低位加 1，当年低位满 100 会向年高位进 1，设计正确。

#### 4.1.7 设置模块

 


图 27 设置分钟仿真图

 


图 28 设置小时仿真图

 


图 29 设置月份仿真图

 


图 30 设置年低位仿真图

由上面的仿真图可以看出，k1 能选择设置的时间，k2 增加控制的时间，同时 led 也会根据设置的时间而改变，设计成功。

4.1.8 闹钟模块



图 31 闹钟模式仿真图

由上面仿真图可以看出，当时钟上升沿到来，闹钟设定时间和计数时间相同时，闹钟模块有输出，设计正确。

4.2 实验结果

 


图 32 时分秒计时模式图

 


图 33 年月日计时模式图



 


图 34 设置分钟图

 


图 35 设置小时图

 


图 36 设置日图

 


图 37 设置月份图

 


图 38 设置年低位图

 


图 39 设置年高位图



 


图 40 设置闹钟图

 


图 41 闹钟提醒图

## 五、课程设计总结

通过这次的课程设计我们受益良多，学习到了很多在课堂上没有发现的知识。因为编程是动手实践的学科，通过这样的课程设计，不仅有助于我们巩固课堂上学习到的 VHDL 的理论知识，同时也锻炼了我们把学习到的理论知识用到生活中的能力。

这次万年历的设计，采用了模块化的设计思想，所以才设计过程中，整体思路清晰，后期修改代码，增加新的模块也相对容易，让我们体会到这种编程方式的优点。同时，VHDL 这种软硬件相结合的编程方式，有利于自顶向下地进行设计，而不用考虑太多底层的实现，提高了我们开发的效率。

在测试过程中，天数计数器上出现了比较多的问题。因为存在 4 种情况，在用计数是很容易混淆出错。我们的一个错误就是，闰年有 29 天，因为计数用的变量是 16 位的，而显示的是 10 进制的数，在设计 29 进制计数器时，把判断的阈值设为 30，但实际情况不会出现 0，所以无法在计数到 30 时置零进位。判断的阈值应为 3A。

在设计的过程中，闹钟的时间判定模块原本采用时、分与闹钟的时、分触发进程，结果闹钟会在设定的时间响之后依旧会再响两次。之后改用系统时钟上升沿触发便解决了问题。